# SNAP AND SWITCH (S.A.S)

**Submitted By** POORNESH RAVAL(15BEE090)

ELECTRICAL ENGINEERING DEPARTMENT INSTITUTE OF TECHNOLOGY NIRMA UNIVERSITY March-2017

### **SNAP AND SWITCH (S.A.S)**

#### **Idea Lab Project**

## Under the mentorship of **Prof. V.M.Dholakiya**



## ELECTRICAL ENGINEERING DEPARTMENT INSTITUTE OF TECHNOLOGY NIRMA UNIVERSITY

**March-2017** 

#### **Declaration**

I do hereby declare that the technical project report submitted is original, and is the outcome of the independent investigations/research carried out by me and contains no plagiarism. The research is leading to the discovery of new facts/techniques/correlation of scientific facts already known. This work has not been submitted to or supported by any other University or funding agency.

I do hereby further declare that the text, diagrams or any other material taken from other sources have been acknowledged, referred and cited to the best of our knowledge and understanding.

Date	,
Daw.	•

Place:

Poornesh Raval 15BEE090

Prof. V.M. Dholakiya

Asst. Prof.

#### INSTITUTE OF TECHNOLOGY

#### **IDEA LAB**

#### ELECTRICAL ENGINEERING DEPARTMENT

Final Report of the work done on the Idea Lab Project.

- 1. Project Title: SNAP AND SWITCH (S.A.S)
- 2. Period of Project:
- 3. (a) Name of Student Poornesh Raval(15BEE090) Department – Electrical Engineering
  - (b) Name of Mentor Prof. V.M.Dholakiya Department – Electrical Engineering
- 4. Project Start Date:
- 5. (a) Total Amount Approved 3,000/- (b) Total Expenditure
  - (c) Report of work done
    - i. Brief objective of the project: This project aims at designing a gadget which can turn on or off any electronic device which is plugged in
    - ii. Work done:

Stimulation of the both transmission and receiver module of the device, the entire transmission module with Arduino program and receiver circuit on breadboard.

- iii. Objectives not achieved Synchronization between the transmitter and receiver module.
- iv. Technical difficulties faced synchronizing the transmitter and receiver frequency.

Poornesh Raval 15BEE090 Prof. V.M.Dholakiya
Asst. Professor
Electrical Engg. Department
Institute of Technology,
Nirma University, Ahmedabad

Prof. P. N. Kapil Idea Lab Co-ordinator, Electrical Engg. Department Institute of Technology, Nirma University, Ahmedabad

Dr. Ankit Thakkar Idea Lab Co-ordinator, Institute of Technology, Nirma University, Ahmedabad

Dr. P. N. Tekwani

Head of Department, Electrical Engg. Department, Institute of Technology, Nirma University Ahmedabad. Dr. Alka Mahajan

Director,
Institute of Technology,
Nirma University,
Ahmedabad.

#### **Contents**

Declaration	3
1.1 Introduction	7
1.2 Literature Survey	7
1.3 Major Objectives Proposed.	7
1.4 Experimental Setup , Results and Working	8
1.5 Objectives Achieved.	11
1.6 Objectives Not Achieved	13
1.7 Technical Difficulties Faced	13
1.8 Budget Analysis	14
1.9 Conclusion and Future Work	14

#### 1.1

#### Introduction

Home automation and smart gadgets are now one of the most demanding and essential part of human's life. Whenever we hear the word smart it means something innovative and intelligent. This project is on designing of a innovative gadget which can turn on or off any plugged in device with just a snap.

#### 1.2 Literature survey

Automation is now a days need for every individual whether it can be an manufacturing industry or packaging industry or even home automation everywhere we desire to have easiness of any task to be performed .Controlling electrical devices without actually moving is something which everybody might have thought once , this can be attained by using of wireless communication i.e

electromagnetic waves like IR, UV and so on.

IR are very commonly used in almost every electrical and/or electronic device as remote to turn on or off a device. So in this project we will use the same IR with a the same application but in an engineer's way i.e using IR in more user friendly way.

### 1.3 Major Objectives Proposed

This project aims at designing a S.A.S is a device which can be used to SWITCH OR ALTER THE ELECTRICAL STATE OF ANY DEVICE WHICH IS PLUGGED IN THE PLUG.

```
Arduino code for transmitter :
int Threshold ;
void setup()
```

```
serial.begin(9600);
pinMode(13,OUTPUT);
pinMode(A0,INPUT) ;
}
void loop()
{
Threshold = analogRead(A0);
if(Threshold > 400)
{
    digitalWrite(13,HIGH);
}
else
    {
    digitalWrite(13,LOW);
}
```

#### 1.4 Simulation and Results and Working

#### THE WORKING:

S.A.S works on IR signals along with sound sensor with the contribution of arduino .

So when we snap the fingers it create a sound which is detected by our sensor and processed through the board and creates a small interval IR signal which is received by our receiver which is made in such a way that it alters the electrical state of the device and resulting it to turning ON or OFF the device .

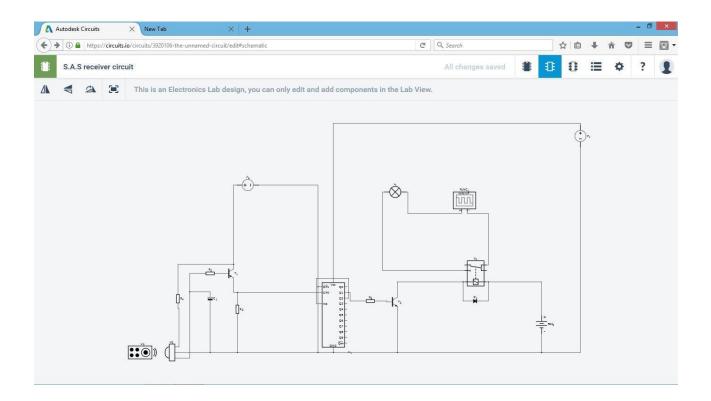


Fig. 1 Schematic circuit diagram of Receiver circuit.

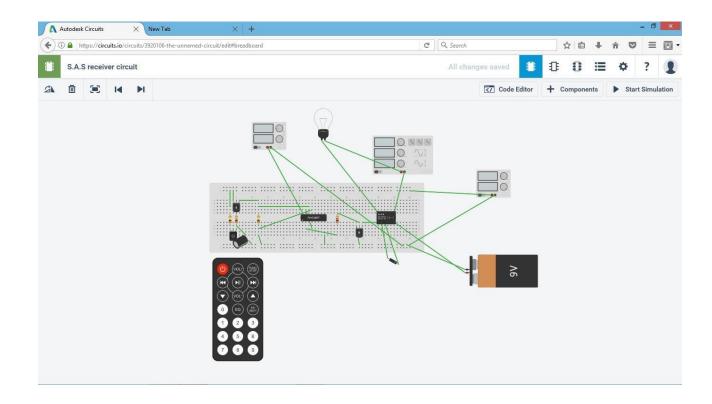


Fig. 2.a Stimulation of receiver circuit (BULB OFF)

The Fig 2.a and Fig 2.b shows the stimulation of the receiver circuit. Fig 2.a shows the receiver side in the absence of IR signal . the bulb or the load remains off .

Fig 2.b shows the receiver side when there is IR signal received by the TSOP1738 and finally the bulb glows.


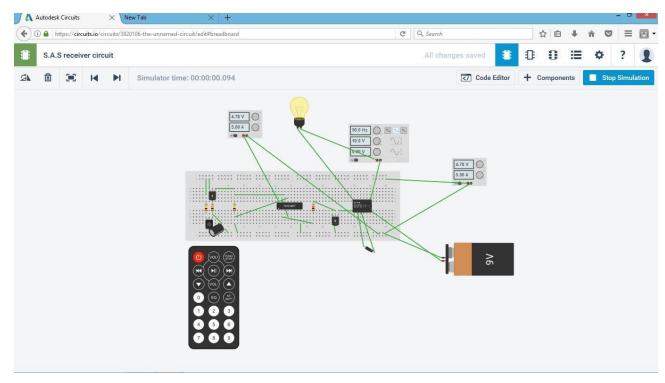



Fig 2.b) Stimulation of Receiver (BULB ON)

#### 1.5 Hardware results and Objectives Achieved

Transmitter using IR , arduino and sound sensor is made.

Receiver module made.

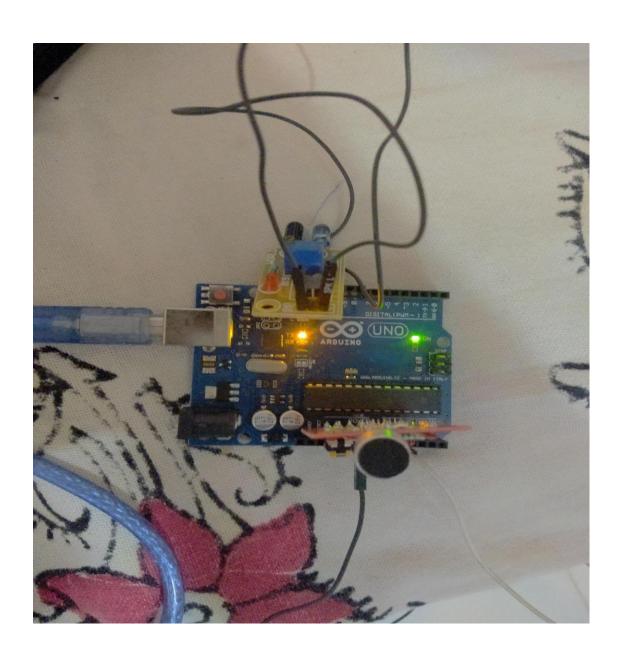

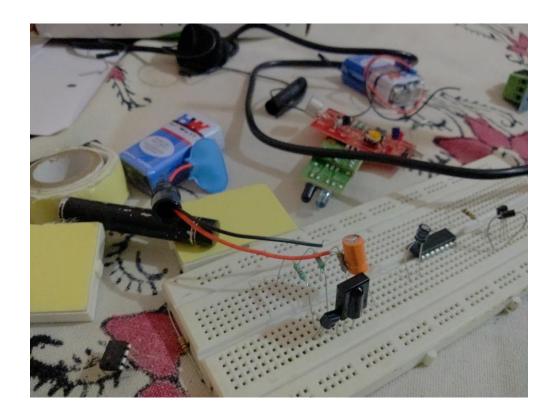

#### 1.6 Objectives not Achieved

Synchronisation between transmitter and receiver, make universal transmitter which allows to control multiple plugged in devices in the room.

#### 1.7 Technical Difficulties Faced

Synchronisation between transmitter and receiver .

#### 1.8 Budget Analysis

1. Budget Sanctioned: Rs. 3,000/-

2. Budget Utilized:

#### 1.9 Conclusion and Future Work

S.A.S can be used everywhere there is plug point and a source of energy and can be used by anyone who don't want to get up and turn the plug switch on or off and of course anyone don't like to stand up and switch the plug.